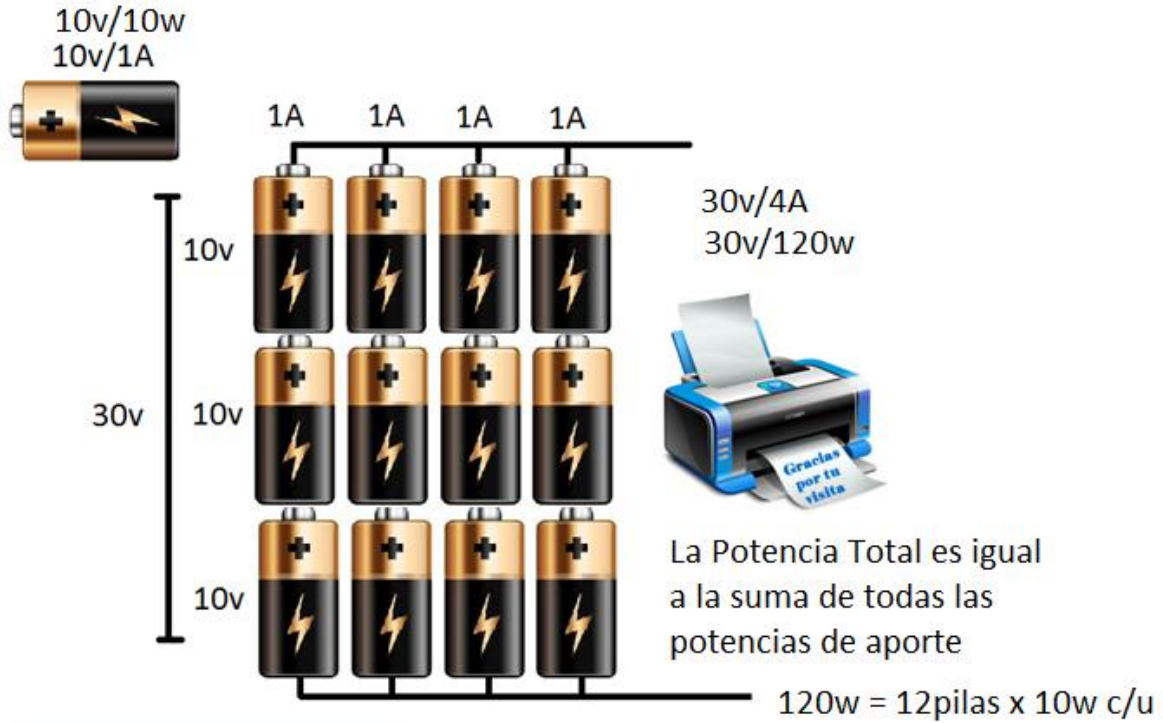


Ejemplo1.



$$I = P/V \quad 1A = 10w/10v$$

$$P = V * I \quad 10w = 10v * 1A$$

$$I = P/V \quad 4A = 120w/30v$$

$$P = V * I \quad 120w = 30v * 4A$$

Ejemplo2.

